

LC memory: stores $E \rightarrow$ gives out later

linear!

$$C \quad q = Cv, \quad C = \frac{\epsilon A}{d} \quad E = KE_0$$

$$i = C \frac{dv}{dt} \quad v = v(t_0) + \frac{1}{C} \int_{t_0}^t i(t') dt' \\ = \frac{1}{C} \int_{-\infty}^t i(t') dt'$$

passive sign conv.

$v \uparrow \rightarrow i \neq 0$; i fin. $\rightarrow v$ cont.

Energy

$$\Delta W = V \Delta q$$


$$W = \int_0^q \frac{q'}{C} dq' = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} CV^2$$

Power

$$P = Vi = V C \frac{dv}{dt}$$

$$\text{Charged } C \quad v(t) = v_0 + \frac{1}{C} \int_0^t i(t') dt'$$

Leakage || w/ R

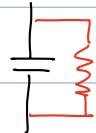

L Solenoid's B leaks on sides, toroid better

[Wb]

$$\phi = \alpha Ni \quad V = N \frac{d\phi}{dt}$$

$$= \alpha N^2 \frac{di}{dt}$$

$\alpha = \frac{\mu A}{l}$ for toroid, where l is the mean core perimeter
and for long solenoid

$$\int_{i(t_0)}^{i(t)} di = \frac{1}{L} \int_{t_0}^t v(t') dt'$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(t') dt'$$

$$E \quad P = i L \frac{di}{dt}$$

$$W = \int_{t_0}^t p(t') dt'$$

$$= \int_0^i L i' di'$$

$$= \frac{1}{2} Li^2$$


Real L series w/ R

Eg. || w/ ①

Combination same as R, not energy though E. initial charge

$$\int \frac{d}{dt} V_{out} = -\frac{1}{RC} \int_0^t V_{in}(t') dt' \quad \left. \right\} \text{find } i(t)$$

$$= -RC \dot{V}_{in}(t)$$

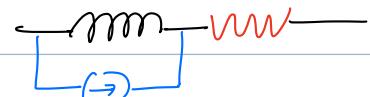

1st order circuits single E storage element (L/C)

$\star C$'s v and L 's i \Rightarrow continuous, \Rightarrow energy

$$RC \quad i_C(t) + i_R(t) = 0$$

$$C \frac{dv_C}{dt} + \frac{V_C}{R} = 0$$

$$\tau \frac{dv_C}{dt} + V_C = 0$$

$$V_C(t) = V_0 e^{-t/\tau}$$

$$RC \equiv \tau \equiv \frac{L}{R}$$

$$RL \quad v_L(t) + v_R(t) = 0$$

$$L \frac{di_L}{dt} + R i_L = 0$$

$$\tau \frac{di_L}{dt} + i_L = 0$$

$$i_L(t) = I_0 e^{-t/\tau}$$

General C/L, compute Reg. relative to C/L

Driven $\frac{RC}{V_R(t) + V_C(t)} = V_s$

$$\tau \frac{dV_C}{dt} + V_C = V_s \quad (\text{w/ } V_C(0) = V_0)$$

$$V_C(t) = (V_0 - V_s) e^{-t/\tau} \quad \text{natural: let } V_s = 0$$

$$+ V_s$$

forced: $V_C(t) = V_s$ is a soln.


$$= V_0 e^{-t/\tau} + V_s (1 - e^{-t/\tau})$$

$\propto V_0$, init

$\propto V_s$, excitation

RL $\tau \frac{di_L}{dt} + i_L = I_s$ parallel
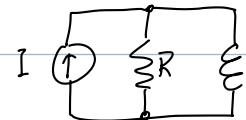
$$i_L(t) = I_s + (I_0 - I_s) e^{-t/\tau}$$



\sum of causes


Linear if $V_0 = 0$, else not lin!

General: 1 cap, any R, indep. source \rightarrow Thevenin, w/ init. V_0 on cap.

\sim var: superposition of indep. source & $V_C(t)$, $y(t) = Y_F + (y_0 - Y_F) e^{-t/\tau}$

Steady-state $y(t) \rightarrow Y_F$, \rightarrow open, \rightarrow short


(w/ \square , τ can < 0 , unstable)

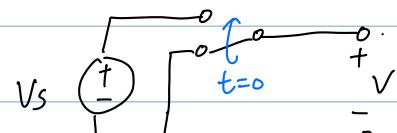


Switch $V_C(0^-) = V_C(0^+)$. Other quantities may not cont.

Step function $u(t - t_0)$

Rec. pulse $u(t - t_1) - u(t - t_2)$

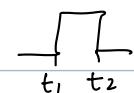

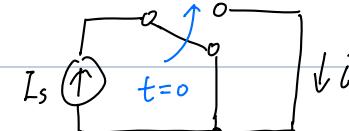\square V linearly blows up, marginally stable



+1 $\frac{1}{L} \frac{di}{dt}$ parasitic
-1 $\frac{1}{C} \frac{dv}{dt}$

E - V_s i_L R_1 R_2 V_{out} H-V pulse generator, $V_{out} = -\frac{R_2}{R_1} V_s$

S make-before-break switch to maintain i .

2nd order circuit

LC V_C, i_L oscillates forever

Parallel RLC $\left\{ \begin{array}{l} V_C = L \frac{di_L}{dt} \\ C \frac{dV_C}{dt} + \frac{V_C}{R} + i_L = 0 \end{array} \right.$

RT, loss ↓ $\left\{ \begin{array}{l} V_C = L \frac{di_L}{dt} \\ C \frac{dV_C}{dt} + \frac{V_C}{R} + i_L = 0 \end{array} \right.$

$\Rightarrow \text{①: } LC \frac{d^2V_C}{dt^2} + \frac{1}{R} \frac{dV_C}{dt} + V_C = 0$

$\ddot{V}_C + \frac{1}{RC} \dot{V}_C + \frac{1}{LC} V_C = 0$


$\ddot{V}_C + 2\alpha \dot{V}_C + \omega_0^2 V_C = 0$

KVL

KCL

$V_C(0) = V_0$

$i_L(0) = I_0$

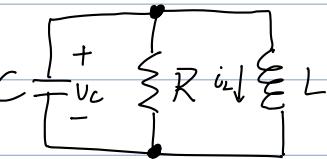

$\text{④} \Rightarrow \text{② } C V_C(0) + \frac{V_0}{R} + I_0 = 0$

$\dot{V}_C(0) = -\frac{1}{C} (I_0 + \frac{V_0}{R})$

General: $\ddot{y} + 2\alpha \dot{y} + \omega_0^2 y = 0$

$\left. \begin{array}{l} y(0) = Y_0 \\ \dot{y}(0) = D_0 \end{array} \right\} (\lambda^2 + 2\alpha\lambda + \omega_0^2) A e^{\lambda t} = 0$

$\lambda_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$

$\lambda_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$

$y(t) = A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}$

$\alpha^2 - \omega_0^2 > 0 \quad R < \frac{1}{2} \sqrt{\frac{L}{C}}$

$y = A_1 e^{\lambda_1 t} + A_2 e^{\lambda_2 t}$

$y(0) = A_1 + A_2$
 $\dot{y}(0) = \lambda_1 A_1 + \lambda_2 A_2$
 $y(0) = A_2$
 $\dot{y}(0) = A_1 - \alpha A_2$

overdamped

$\alpha^2 - \omega_0^2 = 0 \quad R = \frac{1}{2} \sqrt{\frac{L}{C}}$

$y = (A_1 t + A_2) e^{-\alpha t}$

critically damped

$\alpha^2 - \omega_0^2 < 0 \quad R > \frac{1}{2} \sqrt{\frac{L}{C}}$

$y = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$ underdamped

$y(0) = B_1$

$(\dot{y}(0) = \omega_d B_2 - \alpha B_1)$

$\omega_d \equiv \sqrt{\omega_0^2 - \alpha^2}$

$i_L \text{ ①} \rightarrow \text{②} \quad \ddot{i}_L + \frac{1}{RC} \dot{i}_L + \frac{1}{LC} i_L = 0 \quad \text{same coeff as } V_C !!$

$\dot{i}_L(0) = \frac{V_0}{L}$ init. differ!

Series RLC

$C \frac{dV_C}{dt} = i_L$

$L \frac{di_L}{dt} + R i_L + V_C = 0$

$i_L(0) = 0$

$i_L(0) = -\frac{1}{L}(V_0 + RI_0)$

$\alpha = \frac{R}{2L}$


$\omega_0 = \frac{1}{\sqrt{LC}}$

Driven parallel

$L \dot{i}_L = V_C$

$C \dot{V}_C + \frac{1}{R} V_C + i_L = I_s$

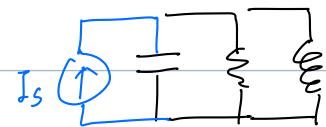$\ddot{i}_L + \frac{1}{RC} \dot{i}_L + \frac{1}{LC} i_L = \frac{1}{LC} I_s$ same init. cond.



Forced: open C, short L, $\rightarrow i_{L,F} = I_s$

so $y(t) = Y_F + y_n(t) \rightarrow 3 \text{ cases, and find coeffs.}$

Series $C \dot{v}_c = i_L$

$$L \dot{i}_L + R i_L + v_c = V_s \rightarrow \ddot{v}_c + \frac{R}{L} \dot{v}_c + \frac{1}{LC} v_c = \frac{1}{LC} V_s$$

Summary 2 indep. elements

Dif circuits may look same when it comes to natural response

Switched $v_c(0^+) = v_c(0^-)$, $i_L(0^+) = i_L(0^-)$

Solve for init cond at 0^- (steady)

Lossless LC ($R \rightarrow \infty$ for parallel)

$$\alpha = 0, \omega_d = \omega_0 = \frac{1}{\sqrt{LC}}$$

App. oscillator, make a $-G$ via transconductor

